

Easy

Deputy Executive Engineer (Electrician)

2026

Gujarat Public Service Commission / Assistant Engineer (Electrical)

Consider the following statements regarding three-phase systems: 1. Total power = $3 V_L I_L \cos \phi$. 2. Power is constant in balanced system. 3. Neutral current

A

1 and 2 only

B

2 and 3 only

C

1 and 3 only

D

1, 2 and 3

Correct

Correct Answer: D

Full Detailed Explanation

Correct Answer: D - 1, 2 and 3 Quick Concept Explanation A balanced three-phase system has three equal-magnitude phase quantities displaced by 120° . For a balanced load, the instantaneous total three-phase power is constant and the phasor sum of phase currents is zero, so a neutral conductor carries no current in the ideal balanced case. Key relation: $P = 3 V_L I_L \cos \phi$. Exam focus: Balanced load $I_R + I_Y + I_B = 0$. Common trap: Do not apply zero-neutral-current result to unbalanced or harmonic-rich loads. Statement-wise Verification Statement 1 - Correct. Total power = $3 V_L I_L \cos \phi$. $P = 3 V_L I_L \cos \phi$. Statement 2 - Correct. Power is constant in balanced system. For a balanced load, the instantaneous total three-phase power is constant and the phasor sum of phase currents is zero, so a neutral conductor carries no current in the ideal balanced case. Statement 3 - Correct. Neutral current is zero in balanced load. For a balanced load, the instantaneous total three-phase power is constant and the phasor sum of phase currents is zero, so a neutral conductor carries no current in the ideal balanced case. Core Concept A balanced three-phase system has three equal-magnitude phase quantities displaced by 120° . For a balanced load, the instantaneous total three-phase power is constant and the phasor sum of phase currents is zero, so a neutral conductor carries no current in the ideal balanced case. Formula / Key