

Medium

Deputy Executive Engineer (Electrician)

2026

Gujarat Public Service Commission / Assistant Engineer (Electrical)

Consider the following statements regarding Resonance in RLC Circuit: 1. In series resonance, impedance becomes minimum and current becomes maximum. 2. At resonance,

A

2 and 3 only

B

1 and 4 only

C

1, 2 and 3 only

Correct

D

All of the above

Correct Answer: C

Full Detailed Explanation

Correct Answer: C - 1, 2 and 3 only Quick Concept Explanation For a series RLC circuit, $X_L = X_C$ at resonance, so the impedance is purely resistive and minimum, current is maximum, and power factor is unity. In an ideal parallel resonant circuit the input impedance is high, not minimum.

Key relation: $Z = \frac{1}{\sqrt{\frac{1}{R^2} + (\frac{1}{X_C} - \frac{1}{X_L})^2}}$; $f = \frac{1}{2\pi\sqrt{LC}}$; at resonance $X_L = X_C$. Exam focus: Series resonance: Z minimum, I maximum. Parallel resonance: input Z maximum (ideal case). Common trap: Reactive voltages can be large even though net reactive voltage is zero. Statement-wise Verification Statement 1 - Correct. In series resonance, impedance becomes minimum and current becomes maximum. For a series RLC circuit, $X_L = X_C$ at resonance, so the impedance is purely resistive and minimum, current is maximum, and power factor is unity. Statement 2 - Correct. At resonance, inductive reactance equals capacitive reactance. $Z = \frac{1}{\sqrt{\frac{1}{R^2} + (\frac{1}{X_C} - \frac{1}{X_L})^2}}$; $f = \frac{1}{2\pi\sqrt{LC}}$; at resonance $X_L = X_C$. Statement 3 - Correct. Power factor at resonance becomes unity. For a series RLC circuit, $X_L = X_C$ at resonance, so the impedance is purely resistive and minimum, current is maximum, and power factor is unity. Statement 4 - Incorrect. In parallel resonance, impedance becomes minimum. The correct principle is: For a series RLC circuit, $X_L = X_C$ at resonance, so the impedance is purely resistive and minimum, current is maximum, and power factor is unity. Core