

Easy

Deputy Executive Engineer (Electrician) 2026

Gujarat Public Service Commission / Assistant Engineer (Electrical)

A circuit contains two independent voltage sources connected with resistors. Then 1. Superposition considers one independent source at a time. 2. Total current is sum of

A

1, 2 and 4 only

Correct

B

1 and 3 only

C

2 and 3 only

D

All of the above

Correct Answer: A

Full Detailed Explanation

Correct Answer: A - 1, 2 and 4 only
Quick Concept Explanation Superposition is a linear-circuit method used to find voltages or currents caused by multiple independent sources. Analyze one independent source at a time, replace other independent voltage sources by shorts and independent current sources by opens, and keep dependent sources active. Key relation: $x = x_1 + x_2 + \dots$ for a linear response; $P = V^2/R = I^2 R$ is not a superposable quantity. Exam focus: Deactivate only independent sources; never suppress a dependent source. Common trap: Adding powers from separate source cases is a classic trap. Statement-wise Verification Statement 1 - Correct. Superposition considers one independent source at a time. Analyze one independent source at a time, replace other independent voltage sources by shorts and independent current sources by opens, and keep dependent sources active. Statement 2 - Correct. Total current is sum of individual source contributions. Power is nonlinear in voltage/current and therefore individual power contributions are not directly added. Statement 3 - Incorrect. Power can be directly added from individual source contributions. Superposition applies to linear voltage/current responses; power is quadratic and cannot be summed from isolated-source powers Statement 4 - Correct. Dependent sources remain active in analysis. Analyze one independent source at a time