

Medium

Deputy Executive Engineer (Electrician)

2026

Gujarat Public Service Commission / Assistant Engineer (Electrical)

A two-port network has defined Z-parameters. Then 1. Defined under open-circuit conditions. 2. Z_{11} represents input impedance. 3. Z_{12} represents transfer

A**All of the above****Correct****B**

1 and 4 only

C

2 and 3 only

D

1, 2 and 3 only

Correct Answer: A

Full Detailed Explanation

Correct Answer: A - All of the above

Quick Concept Explanation For a linear two-port, terminal voltages are expressed in terms of terminal currents. Open-circuiting a port forces its current to zero and isolates the required coefficient. Key relation: $V_1 = Z_{11} I_1 + Z_{12} I_2$; $V_2 = Z_{21} I_1 + Z_{22} I_2$. $Z_{11} = (V_1/I_1)|_{I_2=0}$, $Z_{12} = (V_1/I_2)|_{I_1=0}$. Exam focus: Memorize the condition Z open circuit ($I=0$) and Y short circuit ($V=0$). Common trap: Do not label $Z_{12}=Z_{21}$ as symmetry; that equality is the reciprocity condition.

Statement-wise Verification

Statement 1 - Correct. Defined under open-circuit conditions. Z-parameters are determined using open-circuit conditions because the defining current at the other port is set to zero.

Statement 2 - Correct. Z_{11} represents input impedance. $Z_{11} = V_1/I_1$ with $I_2=0$, so it is the driving-point/input impedance at port 1 under output open circuit.

Statement 3 - Correct. Z_{12} represents transfer impedance. $Z_{12} = V_1/I_2$ with $I_1=0$ is a transfer impedance (reverse transfer impedance in the usual port convention).

Statement 4 - Correct. Can be used in network interconnections. Two-port parameter sets are used to analyze interconnected networks; Z-parameters are especially convenient for series-type interconnections and general two-port modeling.

Core Concept For a linear two-port, terminal voltages are expressed in terms of terminal currents. Each Z