

Easy

Deputy Executive Engineer (Electricity) 2026

Ports Authority of Gujarat / Assistant Engineer (Electrical)

-

- A

1, 2, 3
- B

2, 3
- C

1, 3
- D

1, 2, 3

Correct

Correct Answer: D

Full Detailed Explanation

: - 1, 2, 3

120

: $P = \sqrt{3} V_L I_L \cos \phi$
 $I_R + I_Y + I_B = 0.$

1

$= \sqrt{3} V_L I_L$