

Easy

Deputy Executive Engineer (Electricity)

2026

Ports Authority of Gujarat / Assistant Engineer (Electrical)

Consider the following statements regarding Logic Gates: 1. NAND and NOR gates are universal gates capable of implementing any Boolean function. 2. XOR gate

A

1 and 2 only

B

1 and 3 only

C

2 and 3 only

D

1, 2 and 3

Correct

Correct Answer: D

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/gu/question/universal-gates-and-algebraic-properties/>