

Easy

Deputy Executive Engineer (Electricity) 2026

Uttar Pradesh Power Corporation Limited / Assistant Engineer (Electrical) 2026

,

- A

1 3
- B

2 3
- C

1 2

Correct
- D

1, 2 3

Correct Answer: C

Full Detailed Explanation

: C - 1 2

$I_1/I_2=N_2/N_1=1/a;$ $V_1I_1=V_2I_2.$: $V_1/V_2=N_1/N_2=a;$

;