

Hard

Assistant Engineer (Electrical), Class-2 2025

Building Department

V_{AB} $i_{AB} = 5\text{ A}$.

- A

32.76V
- B

35.56V
- C


36.12V
- D

34.21

Correct

Correct Answer: D

Full Detailed Explanation

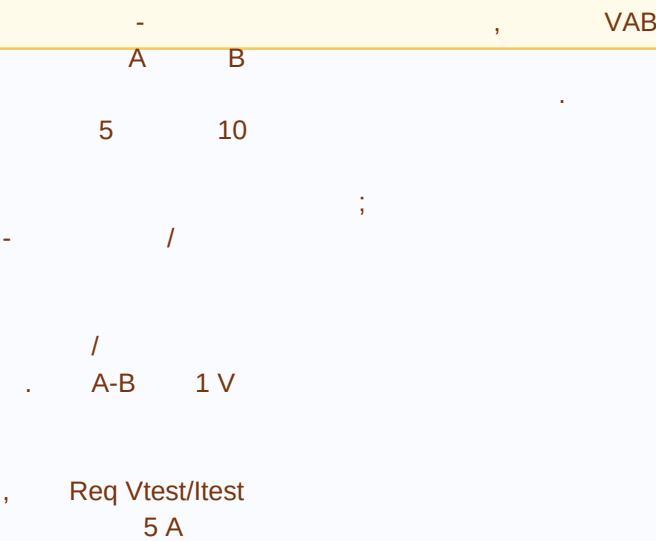

Open live question on website:

<https://sarkariresultout.com/pyq/gu/question/gpsc-ae-electrical-q116-equivalent-resistance-and-terminal-voltage/>