

Easy

Assistant Engineer (Electrical), Class 2025

Building Department

How many inputs are required for a 1-of-10 BCD decoder?

A

4

Correct

B

8

C

10

D

2

Correct Answer: A

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/gu/question/gpsc-ae-electrical-q156-bcd-to-decimal-decoder-inputs/>