

Hard

Assistant Engineer (Electrical), Class 2025

Building Department

A step-down delta-star transformer, with per-phase turns ratio of 5, is fed from a 3-phase, 1100 V, 50 Hz source. The secondary of this transformer through a 3-pulse

A

2 22 A

Correct

B

1 11 A

C

2 11 A

D

1 22 A

Correct Answer: A

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/gu/question/gpsc-ae-electrical-q166-maximum-load-current-from-delta-star-transformer/>