

Easy

Assistant Engineer (Electrical), Class 2025

Building Department

Time constant of an inductive circuit

A

increases with the increase of inductance and the decrease of **Correct**

B

increases with the increase of inductance and the increase of

C

increases with the decrease of inductance and the decrease of

D

increases with the decrease of inductance and the increase of

Correct Answer: A

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/gu/question/gpsc-ae-electrical-q186-rl-time-constant/>