

Medium

Deputy Executive Engineer (Electricity)

2026

ports Authority of Gujarat / Assistant Engineer (Electrical)

Consider the following statements regarding linear resistive networks: 1. Superposition theorem is applicable only if the network contains independent sources.

A

1 and 2 only

Correct

B

2 only

C

2 and 3 only

D

1, 2 and 3

Correct Answer: A

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/hi/question/superposition-with-dependent-sources/>