

Easy

Deputy Executive Engineer (Electricity) 2026

Uttar Pradesh Power Corporation Limited / Assistant Engineer (Electrical) 2026

: 1.

- A

1, 2, 3
- B

2, 3
- C

1, 3
- D

1, 2, 3

Correct

Correct Answer: D

Full Detailed Explanation

: - 1, 2, 3

$$V_s = I_s R$$

$$I_s = \frac{V_s}{R}$$

$$V_s = I_s R$$

$$I_s = \frac{V_s}{R}$$

/