

Easy

Deputy Executive Engineer (Electricity) 2026

Ports Authority of Gujarat / Assistant Engineer (Electrical)

A circuit contains two independent voltage sources connected with resistors. Then 1. Superposition considers one independent source at a time. 2. Total current is sum of

A

1, 2 and 4 only

Correct

B

1 and 3 only

C

2 and 3 only

D

All of the above

Correct Answer: A

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/hi/question/superposition-of-independent-sources/>