

Easy

Assistant Engineer (Electrical), Class 2025

Building Department

To obtain wide bandwidth, network is designed with which of the following?

A

High Q factor

B

Low Q factor

Correct

C

Unity Q factor

D

Zero Q factor

Correct Answer: B

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/hi/question/gpsc-ae-electrical-q115-q-bandwidth-relationship/>