

Hard

Assistant Engineer (Electrical), Class 2025

Building Department

Find V_{AB} if $i_{AB} = 5 \text{ A}$.

A

32.76V

B

35.56V

C

36.12V

D

34.21V

Correct

Correct Answer: D

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/hi/question/gpsc-ae-electrical-q116-equivalent-resistance-and-terminal-voltage/>