

Moderate

Assistant Engineer (Electrical), Class 2025

Building Department

In non-circulating current mode dual converters, the circulating current is avoided by

A

Connecting a series reactor

B

Maintaining $I_1 + I_2 = 180$

C

Operating only one converter

Correct

D

Adding an extra SCR

Correct Answer: C

Full Detailed Explanation

Open the live question URL below to read the full explanation, related links and practice flow.

Open live question on website:

<https://sarkariresultout.com/pyq/hi/question/gpsc-ae-electrical-q167-non-circulating-current-dual-converter/>